

Lab 2 Simulation Outputs

Convince us that you know how to write appropriately thorough testbenches, you wrote such testbenches, and your implementation of each module functions as it should

Adder

Name	Value	160 ps	170 ps	180 ps	190 ps	200 ps	210 ps	220 ps	230 ps	240 ps	250 ps	260 ps	270 ps	280 ps	290 ps	300 ps	310 ps	320 ps	330 ps	340 ps	350 ps	360 ps	370 ps	380 ps	390 ps	400 ps	410 ps										
> a[5:4:0]	0	0																	1																		
> b[5:4:0]	5	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31	0	1	2	3	4	5	6	7	8	9									
> expect_5[4:0]	5	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31	1	2	3	4	5	6	7	8	9	10									
> sum5[4:0]	5	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31	1	2	3	4	5	6	7	8	9	10									
cout5	0																																				
flag	0																																				
i[31:0]	0	0																	1																		
> k[31:0]	5	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31	0	1	2	3	4	5	6	7	8	9									

First image here, you can see values of a changing with i and values of b changing with k. i and k go up to a value max of 31 since a and b are 5-bit numbers with a max value of 31. So far, cout remains at 0 since the sum has not been greater than 31.

Name	Value	1,160 ps	1,180 ps	1,200 ps	1,220 ps	1,240 ps	1,260 ps	1,280 ps	1,300 ps	1,320 ps	1,340 ps	1,360 ps	1,380 ps	1,400 ps													
> a[5:4:0]	0	3							4																		
> b[5:4:0]	5	20	21	22	23	24	25	26	27	28	29	30	31	0	1	2	3	4	5	6	7	8	9	10	11	12	13
> expect_[5:4:0]	5	23	24	25	26	27	28	29	30	31	32	33	34	4	5	6	7	8	9	10	11	12	13	14	15	16	17
> sum[5:4:0]	5	23	24	25	26	27	28	29	30	31	0	1	2	4	5	6	7	8	9	10	11	12	13	14	15	16	17
cout5	0																										
flag	0																										
> i[31:0]	0	3							4																		
> k[31:0]	5	20	21	22	23	24	25	26	27	28	29	30	31	0	1	2	3	4	5	6	7	8	9	10	11	12	13

In this second image, there are 3 cases where cout is set to 1, and that is due to the sum of a and b being greater than 31. The variable sum may seem incorrect, but if you consider that the decimal value of cout when it is 1 is actually 32 and add the value of the sum var, then it returns the correct result.

Name	Value	7,340 ps	7,360 ps	7,380 ps	7,400 ps	7,420 ps	7,440 ps	7,460 ps	7,480 ps	7,500 ps	7,520 ps	7,540 ps	7,560 ps	7,580 ps													
> a[5:4:0]	0	22			23																						
> b[5:4:0]	5	29	30	31	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22
> expect_5[5:4:0]	5	51	52	53	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
> sum5[5:4:0]	5	19	20	21	23	24	25	26	27	28	29	30	31	0	1	2	3	4	5	6	7	8	9	10	11	12	13
cout5	0																										
flag	0																										
> i[31:0]	0	22			23																						
> k[31:0]	5	29	30	31	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22

In this third image, you can see that there are more cases where cout is set to 1. Notice how the variable flag remains constantly at 0. Flag is only ever set to 1 if the expected value does not match {cout, sum}.

Testbench tcl output:

000 + 000 = 000 -- Expected 000

000 + 001 = 001 -- Expected 001

000 + 002 = 002 -- Expected 002

000 + 003 = 003 -- Expected 0

...

030 + 000 = 030 -- Expected 030

030 + 001 = 031 -- Expected 031


...

Passed 5-bit Addition Test :)

Testbench explanation:

We are convinced that our testbench is thorough and proves we have a properly working adder module because it runs through every possible test case and returns the correct result. This is done by using two nested for loops, one that corresponds to the value of input a and one that corresponds to the value of input b.

Big_Number_First

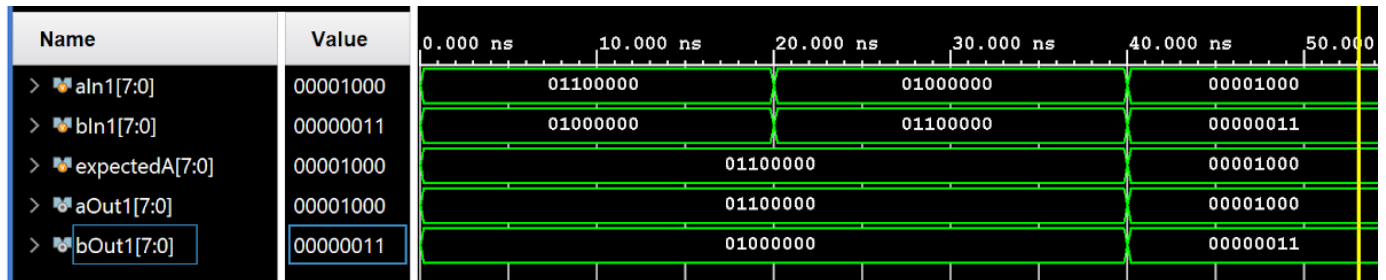

In this image, you can see three test cases being ran. In the first case, a and b have the same mantissa, but different exponents. We expect aIn to be returned as aOut due to it having the larger exponent, and it is.

In the second test case, the values of aIn and bIn are switched so bIn now has the larger exponent. We can see bIn returned as bOut as expected.

The final test case sets aIn and bIn to have the same exponent but different mantissa. bIn actually have a larger mantissa, and overall, is a larger value than aIn. It should still return aIn as aOut because the values of the mantissa are irrelevant in this module and we are only concerned with setting bIn as aOut *only if it has a larger exponent*. Again, our expected matches our output.

Testbench tcl output:

aIn: 01100000, bIn: 01000000, expected aOut: 01100000, actual aOut: 01100000

passed

aIn: 01000000, bIn: 01100000, expected aOut: 01100000, actual aOut: 01100000

passed


aIn: 00001000, bIn: 00000011, expected aOut: 00001000, actual aOut: 00001000

passed

Testbench Explanation:

Our testbench is thorough and provides confidence in our module because we tested for the several different cases we may encounter - aIn's exponent being larger than bIn's, bIn's exponent being larger than aIn's and both aIn and bIn having the same exponent, but bIn having a larger mantissa.

Shifter

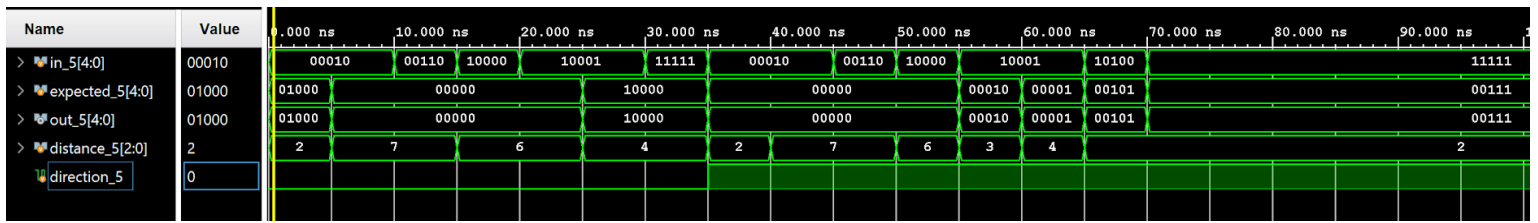

The value of direction indicates whether to shift bits left (set to 0) or right (set to 1). Distance indicates how many places it should be shifted over. Once a value is asked to be shifted past the either edge of the binary number, 0s are put in and it is not seen to “wrap-around.” This is the desired result as an appropriate shift of the mantissa is to be partnered with a different valued exponent in order to return an 8-bit float number that represents the same original value. About half of the cases are tested in the left direction and the other half in the right to cover all bases.


Testbench tcl output:

```
00010 -> 01000, expected 01000
00010 -> 00000, expected 00000
00110 -> 00000, expected 00000
10000 -> 00000, expected 00000
10001 -> 00000, expected 00000
10001 -> 10000, expected 10000
11111 -> 10000, expected 10000
00010 -> 00000, expected 00000
00010 -> 00000, expected 00000
00110 -> 00000, expected 00000
10000 -> 00000, expected 00000
10001 -> 00010, expected 00010
10001 -> 00001, expected 00001
10100 -> 00101, expected 00101
11111 -> 00111, expected 00111
```


Testbench explanation:

The testbench is considered to be thorough as we have tested the possible edge cases in multiple ways with different direction and distances, on top of just having regular different cases. The major key was ensuring proper output when we want to shift the number past the edge and that we don’t just have the number “wrap-around.”

Float_Add

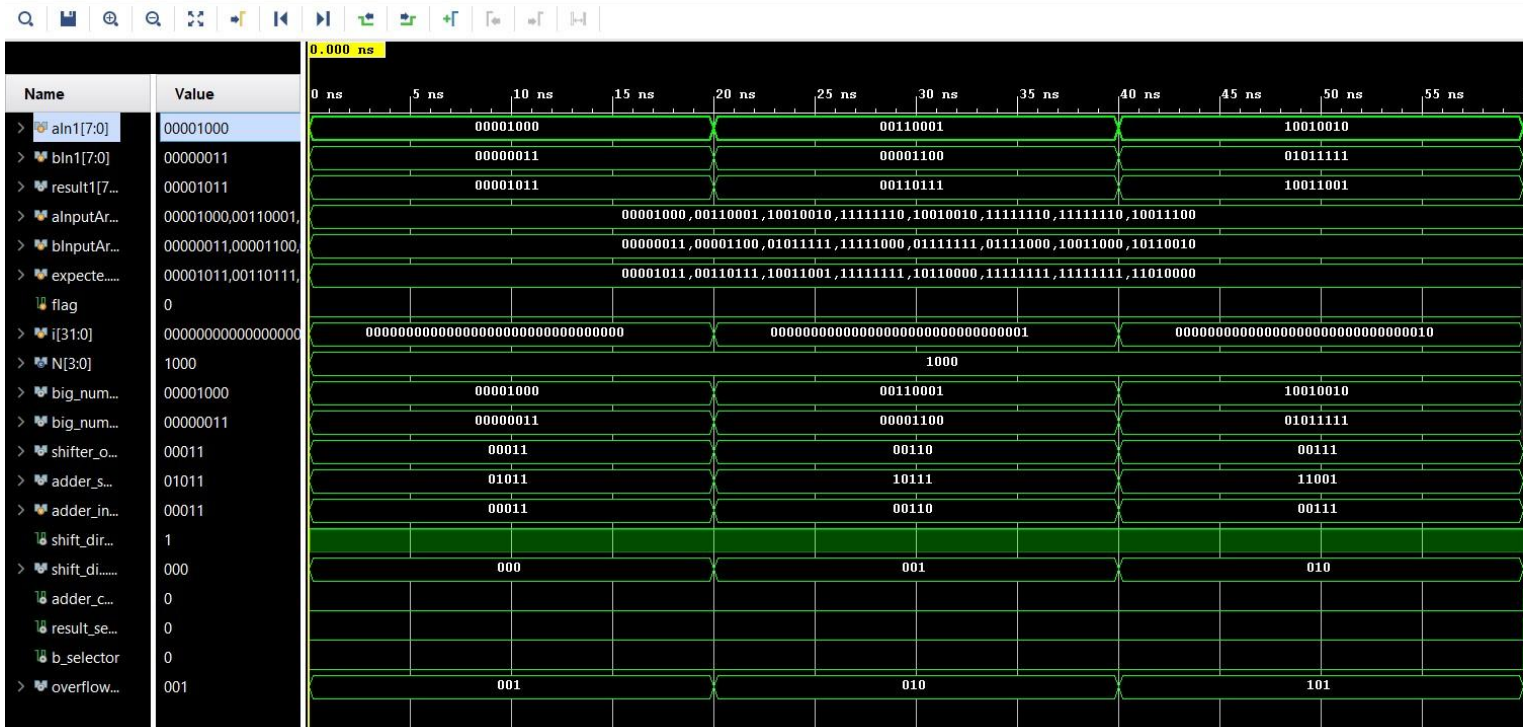

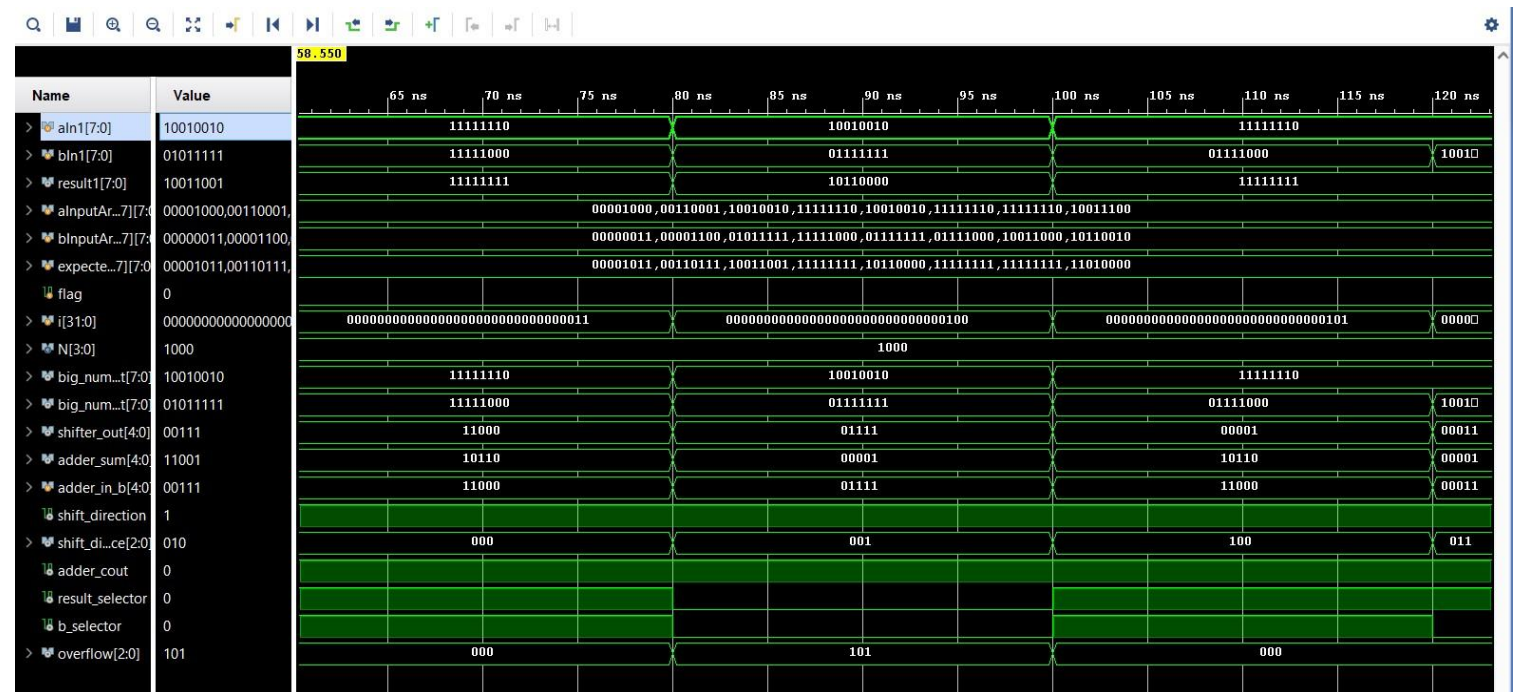The test cases in this image are the ones given in the handout. We can see that the output matches exactly what we were told to expect.



$10010010 + 01111111 = 10110000$, expected = 10110000

$11111110 + 01111000 = 11111111$, expected = 11111111

$11111110 + 10011000 = 11111111$, expected = 11111111

$10011100 + 10110010 = 11010000$, expected = 11010000

Passed float_add Test :)

Testbench explanation:

We believe our testbench is thorough as we have test cases that trigger all possible branches that the logic diagram will need to follow - bIn larger than aIn, input whose sum is larger than what can be possibly represented and will return a saturated output, inputs who after adding the mantissa will return a value that is too large to be held in the mantissa and require the exponent to be increased, and the normal case where the exponent does not have to be changed from what is considered to be the largest exponent and will just concatenate the result from adder with the exponent.